

# Unit 4

## **Combinational Circuit design**

## **Unit 4: Combinational circuit design**

- Combinational circuit design,
- Analysis of CMOS Logic Gates: MOS Device Capacitance, Switching Characteristics,
- Rise Time, Fall Time, Propagation Delay,
- Power Dissipation in CMOS,
- Fan-in, Fan-out,
- Complex Logic Structures,
- static CMOS,
- Ratioed Logic circuits
- Complementary Static CMOS,
- Pseudo NMOS Logic,
- Dynamic CMOS Logic,
- CMOS Domino Logic,
- CMOS Pass Transistor Logic.

# Introduction


---

- Digital logic is divided into
  - combinational and sequential circuits.
- Combinational circuits are those whose outputs depend only on present inputs, while sequential circuits have memory.
- Generally, building blocks for combinational circuits are *logic gates*, while building blocks for sequential circuits are *registers and latches*.
- *Static CMOS* gates use NMOS and PMOS networks to drive 0 and 1 outputs, respectively.
- Majority of circuits use static CMOS because it is robust, fast, energy-efficient, and easy to design.
- But, certain circuits need specific speed, power, or density restrictions that force another solution.
- Such alternative CMOS logic configurations are called *circuit families*.
- Most commonly used alternative circuit families:
  - ratioed circuits,
  - dynamic circuits, and
  - pass transistor circuits.

# Capacitance Estimation

- Switching speed or dynamic response of MOS systems are strongly dependent on parasitic capacitance associated with MOS device and interconnection capacitance which are formed by metal, polysilicon, and diffusion wires in concert with transistor and conductor resistances.
- Total load capacitance on output of a CMOS gate is sum of
  - Gate capacitance
  - Diffusion capacitance
  - Routing capacitance
- To understand source of parasitic capacitance loads and their variations is necessary in design process of a system when performance in terms of speed is a part of design specifications.
- First understand characteristics of an MOS capacitor.
- Then will see MOS transistor gate capacitance, source or drain capacitance and routing capacitance.


# MOSFET Capacitance

 

- Any two conductors separated by an insulator have capacitance
- Gate to channel capacitor is very important
  - Creates channel charge necessary for operation
- Source and drain have capacitance to body
  - Across reverse-biased diodes
  - Called diffusion capacitance because it is associated with source/drain diffusion

 
## MOS Transistor Gate Capacitance Model

Gate capacitance has different components in different modes, but total remains constant.



- Figure shows diagrammatic representation of parasitic capacitance of an MOS transistor
- Where
  - $C_{gs}$  is gate to source capacitance
  - $C_{gd}$  is gate to drain capacitance
  - $C_{sb}$  is source to bulk or substrate diffusion capacitance
  - $C_{db}$  is drain to bulk or substrate diffusion capacitance
  - $C_{gb}$  is gate to bulk capacitance
- Total gate capacitance  $C_g$  of MOS transistor is
- $C_g = C_{gs} + C_{gb} + C_{gd}$
- Behaviour of gate capacitance  $C_g$  of MOS transistor is explained in three regions of operation as



 


Accumulation occurs when  $V_g$  is negative (for P material). Holes are induced under the oxide.

$C_{gate} = C_{ox}A$  where

$$C_{ox} = (\epsilon_{SiO_2} \epsilon_0 / t_{ox})A$$

 
- Where A is area of gate
  - $\epsilon_{SiO_2}$  is dielectric constant or relative permittivity of  $SiO_2$  (Value is 3.9)
  - $\epsilon_0$  is permittivity of free space
  - $t_{ox}$ - oxide layer thickness



Depletion occurs when  $V_g$  is near zero but  $< V_{tn}$ . Here the  $C_{gate}$  is given by  $C_{ox}A$  in series with depletion layer capacitance

$$C_{dep} = (\epsilon_o \epsilon_{Si} / d) A$$

 
- Where  $A$  is area of gate
  - $\epsilon_{SiO_2}$  is dielectric constant of Si (Value is 12)
  - $\epsilon_o$  is permittivity of free space
  - $d$  is depletion layer depth



Inversion occurs when  $V_g$  is positive and  $> V_{tn}$  (for P material). A model for inversion is comprised of  $C_{ox}$  A connecting from gate-to-channel and  $C_{dep}$  connecting from channel-to-substrate.

$$C_{gb} = C_0$$

$$= C_0 * C_{dep} / C_0 + C_{dep}$$

 

Normalized gate capacitance  
versus Gate voltage  $V_{gs}$ .

High freq behavior is due  
to the distributed  
resistance of channel

1. Cut off region where  $V_{gs} < V_t$ .

When MOS device is OFF, no channel so  $C_{gs} = C_{gd} = 0$  and

$C_{gb}$  is modeled as a series combination of two capacitors .e.  $C_o$  and  $C_{dep}$ .

2. Non-saturation or linear region, where  $V_{gs} - V_t > V_{ds}$ .

Channel is formed so  $C_{gs}$  and  $C_{gd}$  (Gate to channel capacitances) will become significant.

They depend on gate voltage.

And values can be found as

$$C_{gd} = C_{gs} = \frac{1}{2} (\epsilon_{SiO_2} \epsilon_o / t_{ox}) A$$

3. Saturation region, where  $V_{gs} - V_t < V_{ds}$ .

Here Channel is heavily inverted. So drain region of channel is pinched off making  $C_{gd} = 0$ . and  $C_{gs}$  will be

$$C_{gs} = \frac{2}{3} (\epsilon_{SiO_2} \epsilon_o / t_{ox}) A$$

Gate capacitance has different components in different modes, but total remains constant.

**TABLE 4.3 Approximation of intrinsic MOS gate capacitance**

Parameter	CAPACITANCE		
	Off	Non-saturated	Saturated
$C_{gb}$	$\frac{\epsilon A}{t_{ox}}$	0	0
$C_{gs}$	0	$\frac{\epsilon A}{2t_{ox}}$	$\frac{2\epsilon A}{3t_{ox}}$
$C_{gd}$	0	$\frac{\epsilon A}{2t_{ox}}$	0 (finite for short channel devices)
$C_g = C_{gb} + C_{gs} + C_{gd}$	$\frac{\epsilon A}{t_{ox}}$	$\frac{\epsilon A}{t_{ox}}$	$\frac{2\epsilon A}{3t_{ox}} \rightarrow \frac{.9\epsilon A}{t_{ox}}$ (short channel)


# Power Dissipation in CMOS

- There are two component that established the amount of power dissipated in CMOS circuit .These are
- Static dissipation due to leakage current or other current drawn continuously from power supply.
- Dynamic dissipation due to
  - ☐ Switching transient current
  - ☐ Charging and discharging of load capacitance
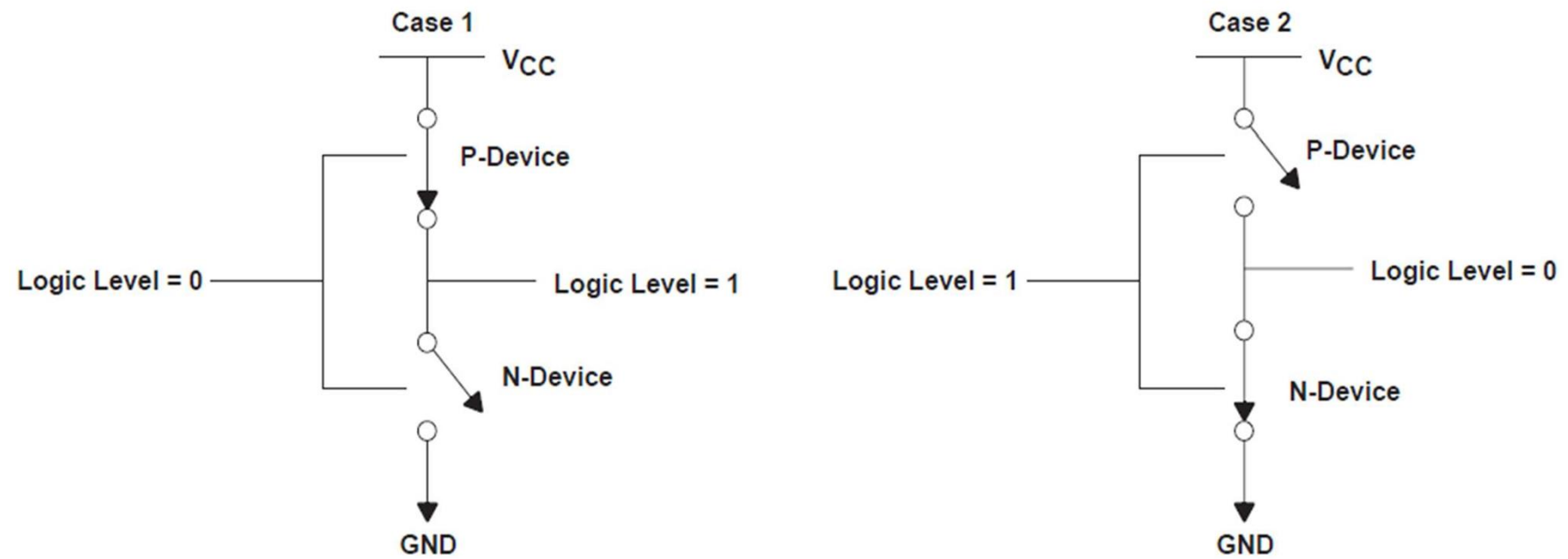
# Static dissipation


- As shown in Figure 1, if input is at logic 0, n-MOS device is OFF, and p-MOS device is ON, output voltage is  $V_{DD}$ , or logic 1.
- Similarly, when input is at logic 1, n-MOS device is biased ON and p-MOS device is OFF, output voltage is GND, or logic 0.
- Note that one of transistors is always OFF when gate is in either of these logic states.
- Since no current flows into gate terminal, and there is no dc current path from VCC to GND, resultant quiescent (steady-state) current is zero, hence, static power consumption ( $P_s$ ) is zero.




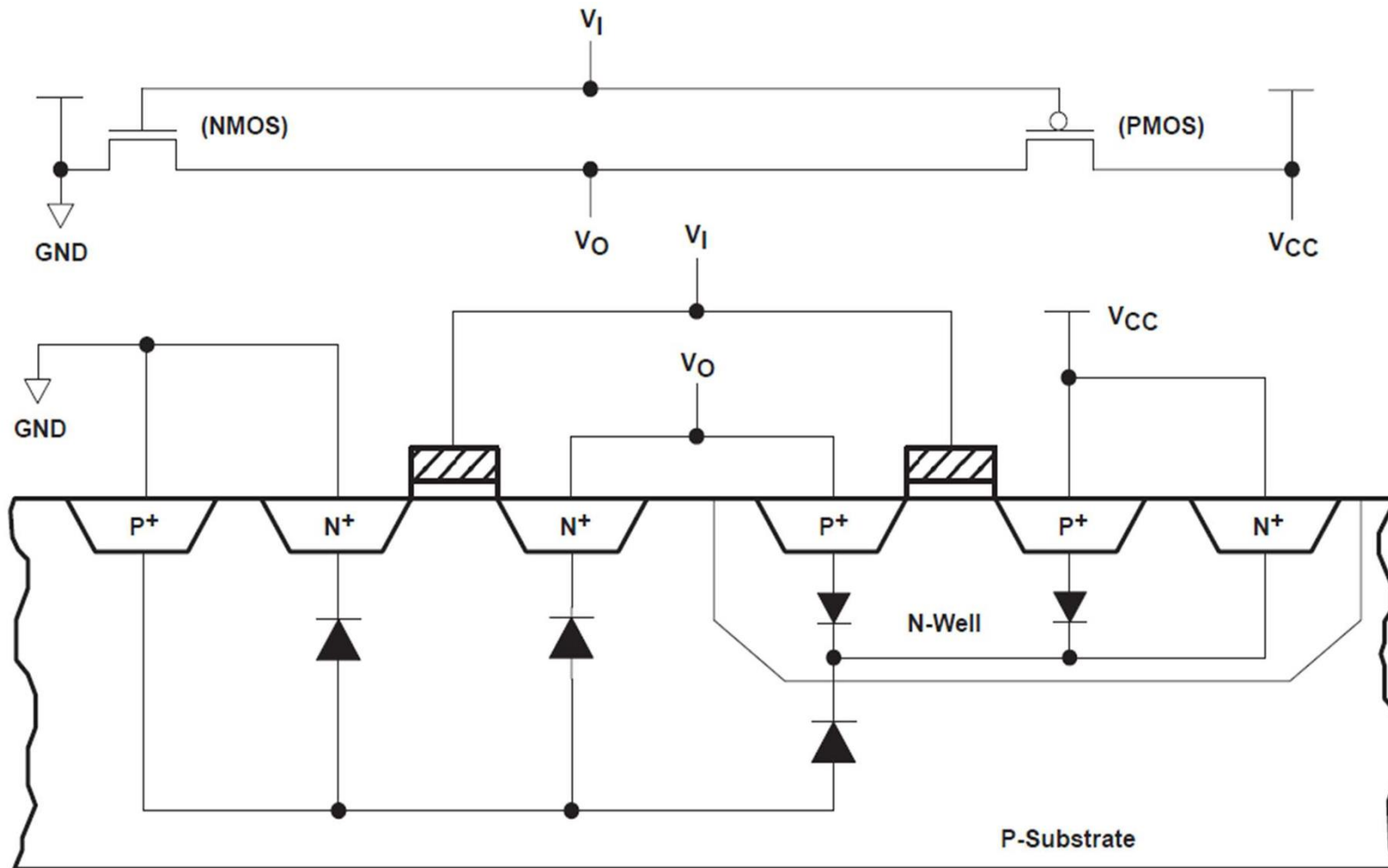
## CMOS Inverter Mode for Static Power Consumption

- But, there is a small amount of static power consumption due to reverse-bias leakage between diffused regions and substrate.
- This leakage inside a device can be explained with a simple model that describes parasitic diodes of a CMOS inverter, as shown below









- Source drain diffusion and N-well diffusion form parasitic diodes.
- Because parasitic diodes are reverse biased, only their leakage currents contribute to static power consumption.
- Leakage current ( $I_0$ ) of diode is described by equation:
- $I_0 = i_s (e^{qV/kT} - 1)$
- Where:
  - $i_s$  = reverse saturation current
  - $V$  = diode voltage
  - $k$  = Boltzmann's constant ( $1.38 \times 10^{-23}$  J/K)
  - $q$  = electronic charge ( $1.602 \times 10^{-19}$  C)
  - $T$  = temperature
- Static power consumption is product of device leakage current and supply voltage.
- Total static power consumption,  $P_s$ , can be obtained as shown in equation below
- $P_s = \Sigma (\text{leakage current}) \times (\text{supply voltage})$



- Leakage current  $I_{CC}$  (current into a device), along with voltage, causes static power consumption in CMOS devices.
- This static power consumption is defined as quiescent, or  $P_S$ , and can be calculated by equation
- $P_S = V_{CC} \times I_{CC}$
- Where:
  - $V_{CC}$  = supply voltage
  - $I_{CC}$  = current into a device (sum of leakage currents)
      
# Dynamic Power Dissipation

- During transition from 0 to 1 or 1 to 0, both PMOS and NMOS are ON for a short period of time. Which results in a short current pulse from  $V_{DD}$  to GND.
- Current is also needed to charge and discharge output load capacitance  $C_L$ .
- Current pulse from  $V_{DD}$  to GND results in a short circuit dissipation which is dependent on **rise/fall time of input, load capacitance  $C_L$  and gate design.**
- Figure shows 3 inverters with varying load from 0pF to 0.2pF with voltage sources to measure currents in SPICE.
- Current flowing in PMOS and NMOS are shown beside each inverter.
- With no load short circuit current is relatively apparent.
- As load capacitance  $C_L$  increases, charge and discharge current starts to dominate current drawn from power supply.



# Power Dissipation: Dynamic

  

# Power Dissipation: Dynamic


## During charging

$$P_{dp} = \frac{1}{t_p} \int_0^{t_1} i_p(t)(VDD - V_o)dt$$

$$i_p(t) = C_L \frac{dV_o}{dt}$$

$$P_{dp} = \frac{C_L}{t_p} \int_0^{VDD} (VDD - V_o)dV_o$$

$$P_{dp} = \frac{C_L}{2t_p} (VDD)^2$$

 




# Power Dissipation: Dynamic

During Discharging

$$P_{dn} = \frac{1}{t_p} \int_{t_1}^{t_p} i_{in}(t) V_o dt$$

$$i_{in}(t) = -C_L \frac{dV_o}{dt}$$
 
$$\begin{aligned} P_{dn} &= \frac{C_L}{t_p} \int_{V_{DD}}^0 -V_o dV_o \\ &= \frac{C_L}{t_p} \frac{V_{DD}^2}{2} \end{aligned}$$



# Power Dissipation: Dynamic

Total Power dissipation

$$\begin{aligned} P_{dp} + P_{dn} &= (C_L / t_p) (V_{DD})^2 \\ &= C_L \cdot f \cdot (V_{DD})^2 \end{aligned}$$

Taking node activity factor  $\alpha$  into consideration:

$$\text{The power dissipation} = \alpha C_L \cdot f \cdot (V_{DD})^2$$

- Where  $\alpha$  is the switching probability or activity factor at the output node (i.e. the average number of output switching events per clock cycle).



# Short circuit Power Dissipation

- Short circuit Power Dissipation is given by
- $P_{sc} = I_{mean} * V_{DD}$

$$P_{sc} = \frac{\beta}{12} (V_{DD} - 2V_t)^3 \frac{t_{rf}}{t_p}$$

- Where  $t_p$  is period of input waveform

  - For input waveform as shown which shows short circuit current for an unloaded inverter



- It shows that short circuit current is dependent on  $\beta(=\mu\epsilon/t_{ox})(W/L)$  and input waveform rise and fall times.
- Slow rise time can result in significant short circuit dissipation for loaded inverters.

# Total power consumption

- The total power consumption of the CMOS inverter is expressed as sum of its three components
  - $P_{\text{total}} = P_s + P_d + P_{\text{sc}}$
  - Where  $P_s$  is Static power consumption
  - $P_d$  is Dynamic power consumption and
  - $P_{\text{sc}}$  is short circuit power consumption

# Static CMOS




Start with network of AND / OR gates

Convert to NAND / NOR + inverters


Push bubbles around to simplify logic

Remember DeMorgan's Law


$$F = \overline{AB + CD}$$

   


(a)

 

(b)

 


(c)

 

(d)

Sketch a design using one compound gate and one NOT gate. Assume  $\sim S$  is available


$$F = D0 \cdot \bar{S} + D1 \cdot S$$

 

# CMOS Logic Structures

---


## CMOS Complementary Logic

 

$$Z = \overline{A * B + C(D + E)}$$
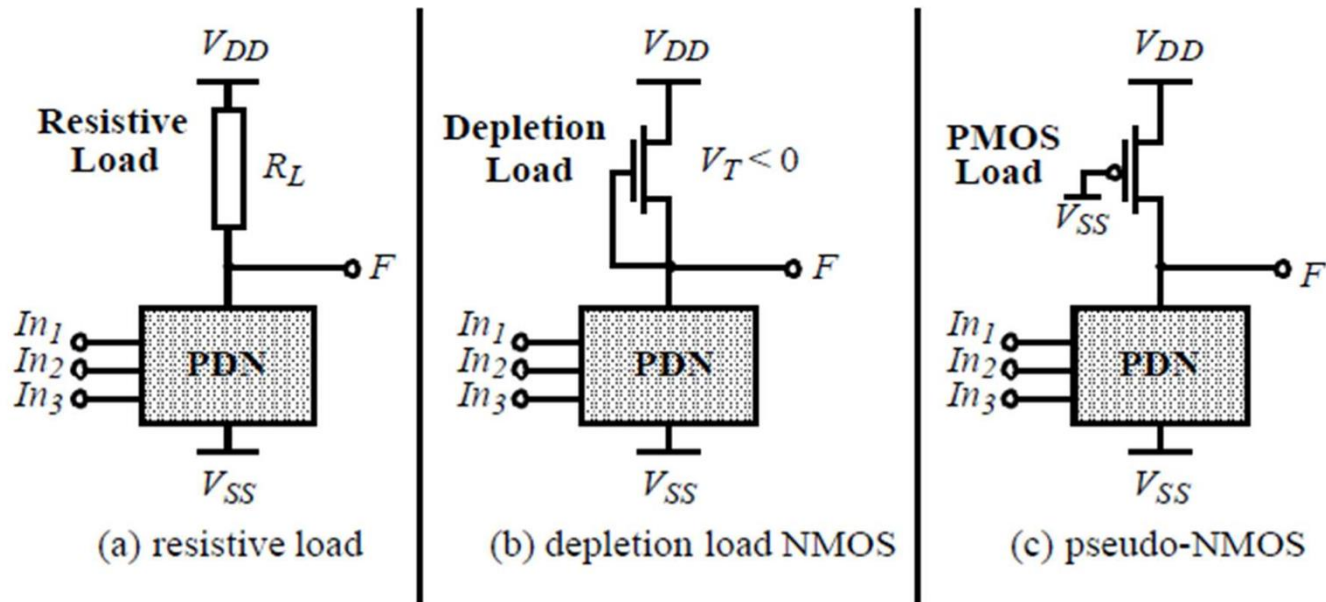
# Ratioed Logic: Concept


- Ratioed logic is an attempt to reduce number of transistors required to implement a given logic function, at cost of reduced robustness and extra power dissipation.
- Purpose of PUN in complementary CMOS is to provide a conditional path between  $V_{DD}$  and output when PDN is turned off.
- In ratioed logic, entire PUN is replaced with a single unconditional load device that pulls up output for a high output.
- Instead of a combination of active pull-down and pull-up networks, such a gate consists of an NMOS pull-down network that realizes logic function, and a simple load device.






# CMOS Logic Structures


## Pseudo-nMOS logic

 


$$F = (A.B) + C.(D+E)$$

 

 Implementation of  $Z = \overline{A \cdot (B + C) + (D \cdot E)}$



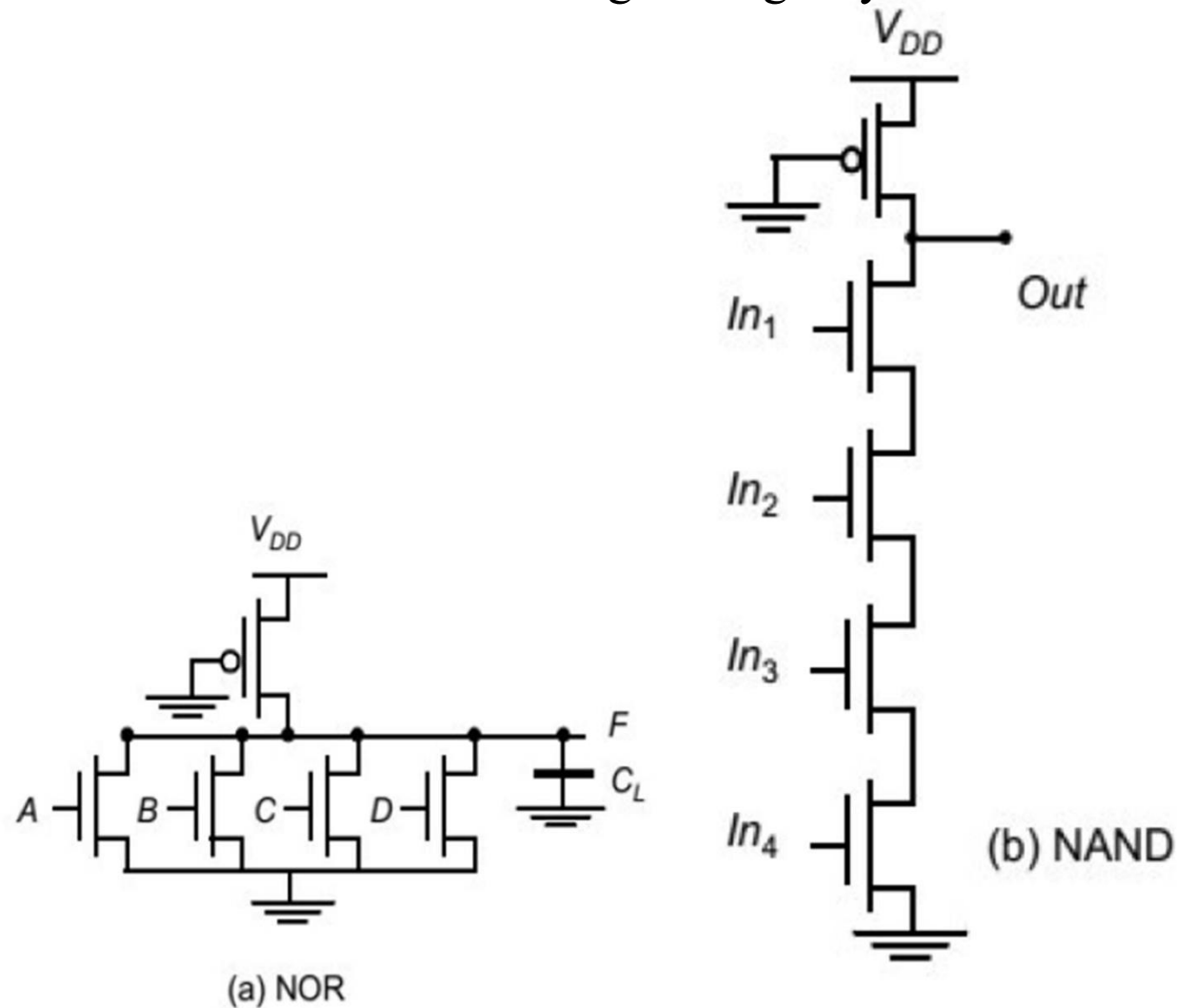
Implementation of 4 input NOR and NAND in pseudo-NMOS logic design style.



Four-input pseudo-NMOS NOR and NAND gates

 
# Dynamic CMOS Logic

- It is designed to avoid static power dissipation with the addition of a clock input



# Dynamic CMOS Logic

$$F = \overline{A * B + C(D+E)}$$

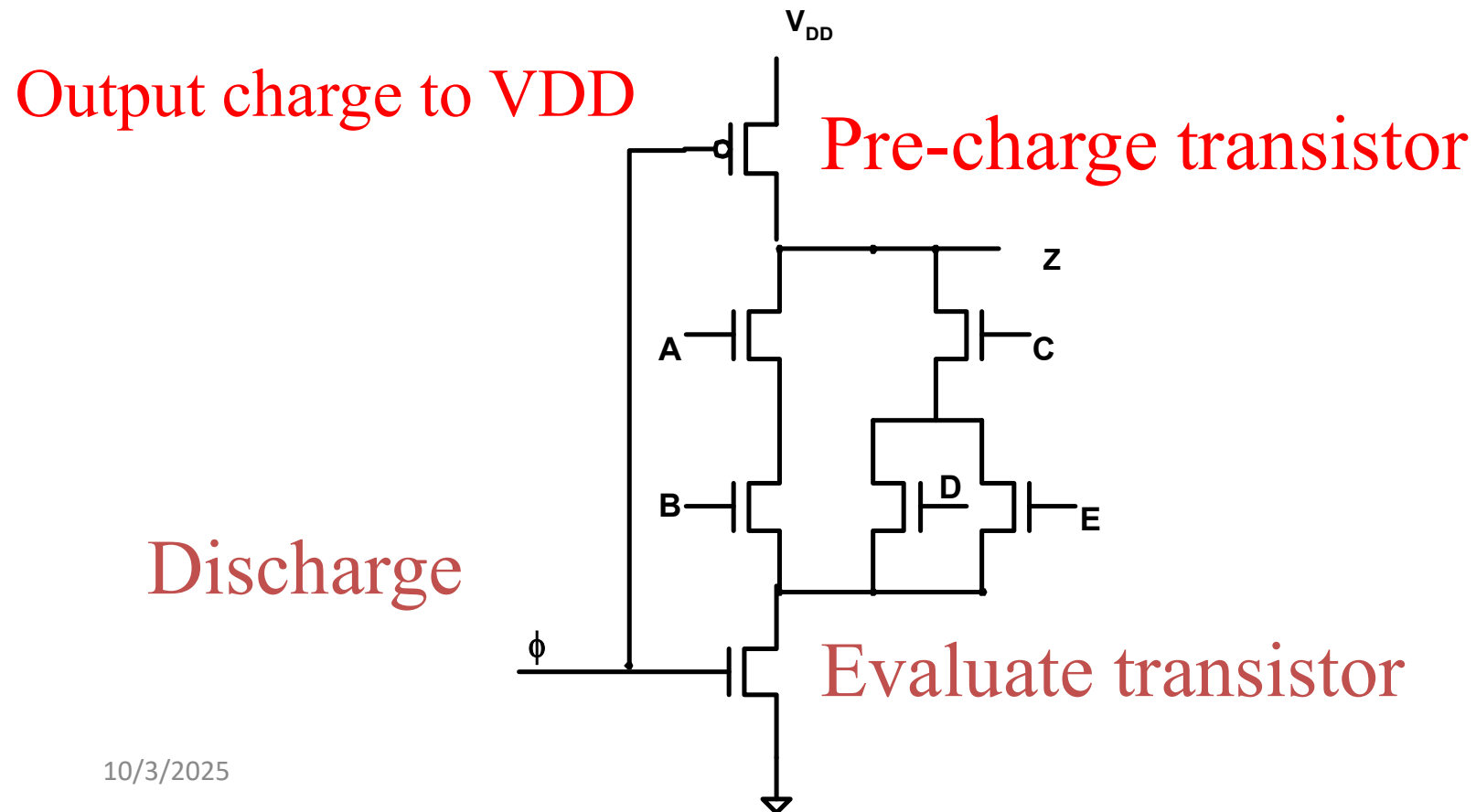

# Dynamic CMOS Logic

---


$$Z = \overline{A * B + C(D+E)}$$

When  $\phi = 1$


Z = High

When  $\phi = 0$

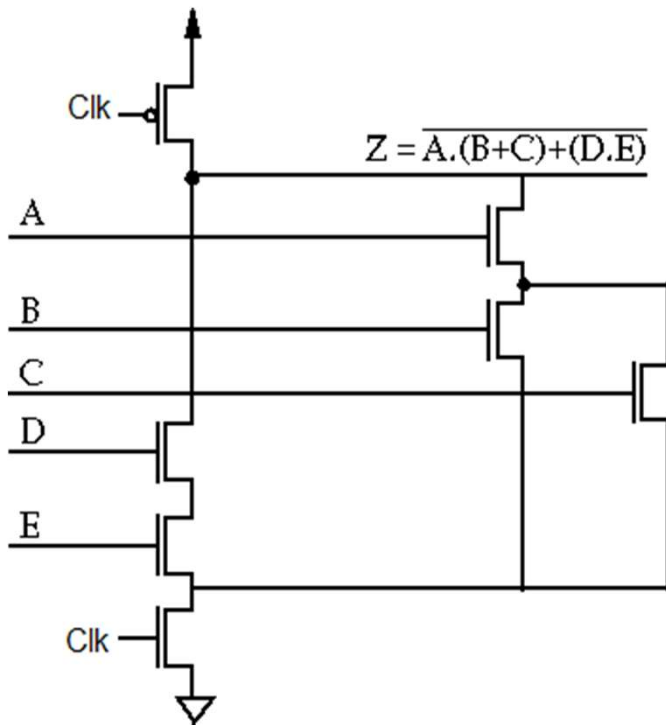
Implementation of  
 $Z = \overline{A.(B+C) + (D.E)}$  i



 Implementation of  
 $Z = \overline{ABC}$




 Implementation of  
 $Z = \overline{AB + C}$



$Z = \overline{A.(B+C) + (D.E)}$  when  $Clk = 1$   
 $Z = HIGH$  when  $Clk = 0$

 
Implementation of  
 $Z = \overline{(A + B) \cdot C}$





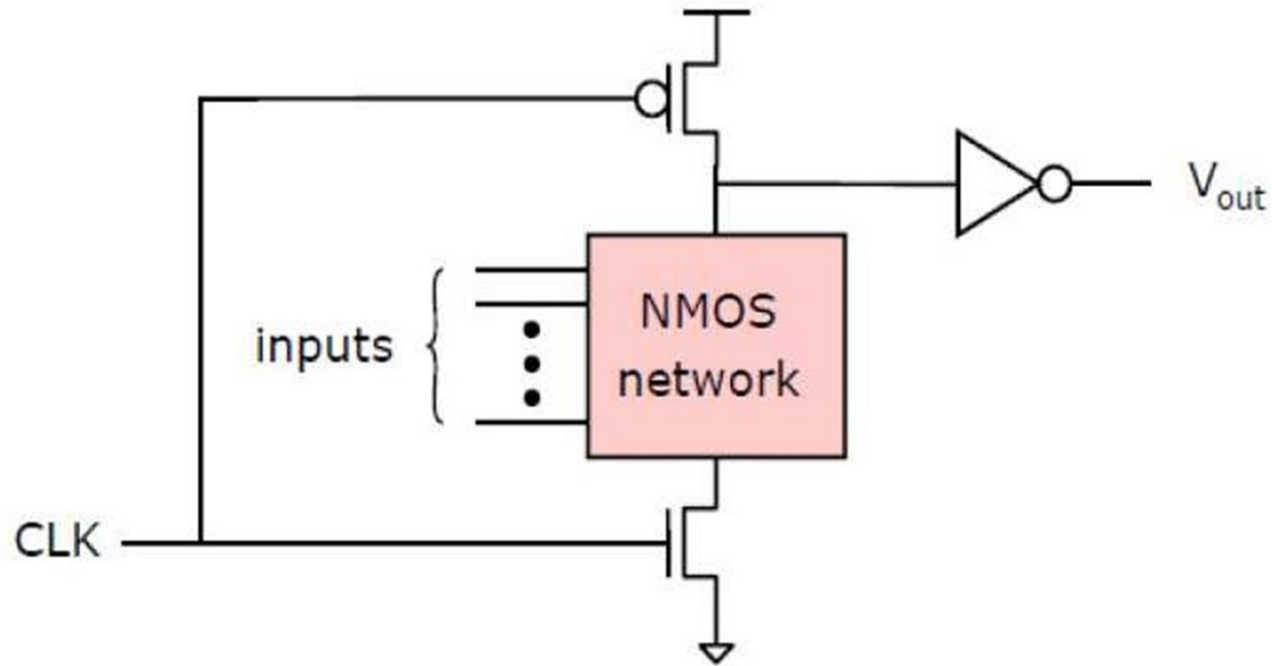
# Domino Logic

- A Domino logic module consists of an n-type dynamic logic block followed by a static inverter.




# Domino Logic

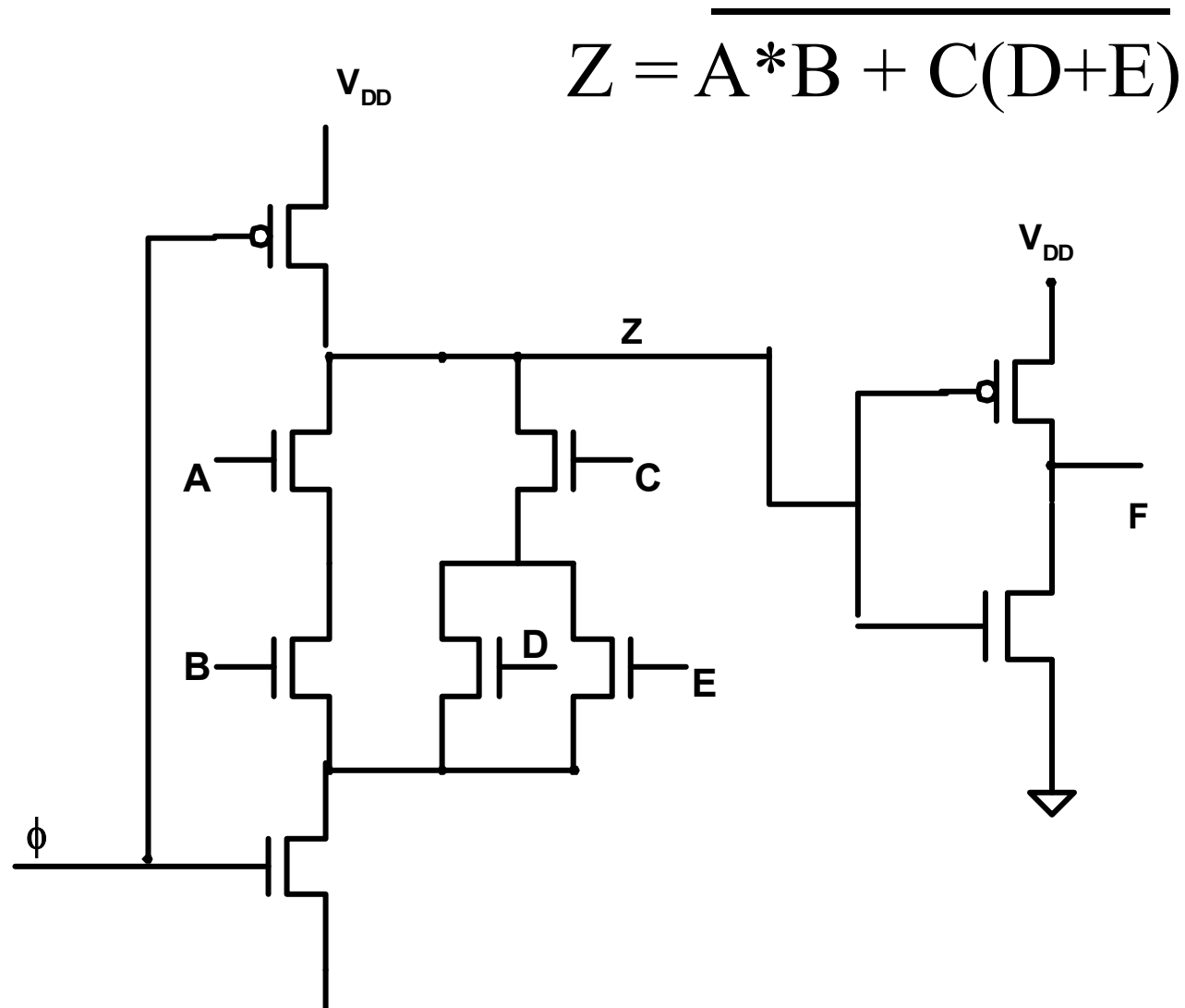





Implementation of

$$Z = \overline{A.(B + C) + (D.E)}$$

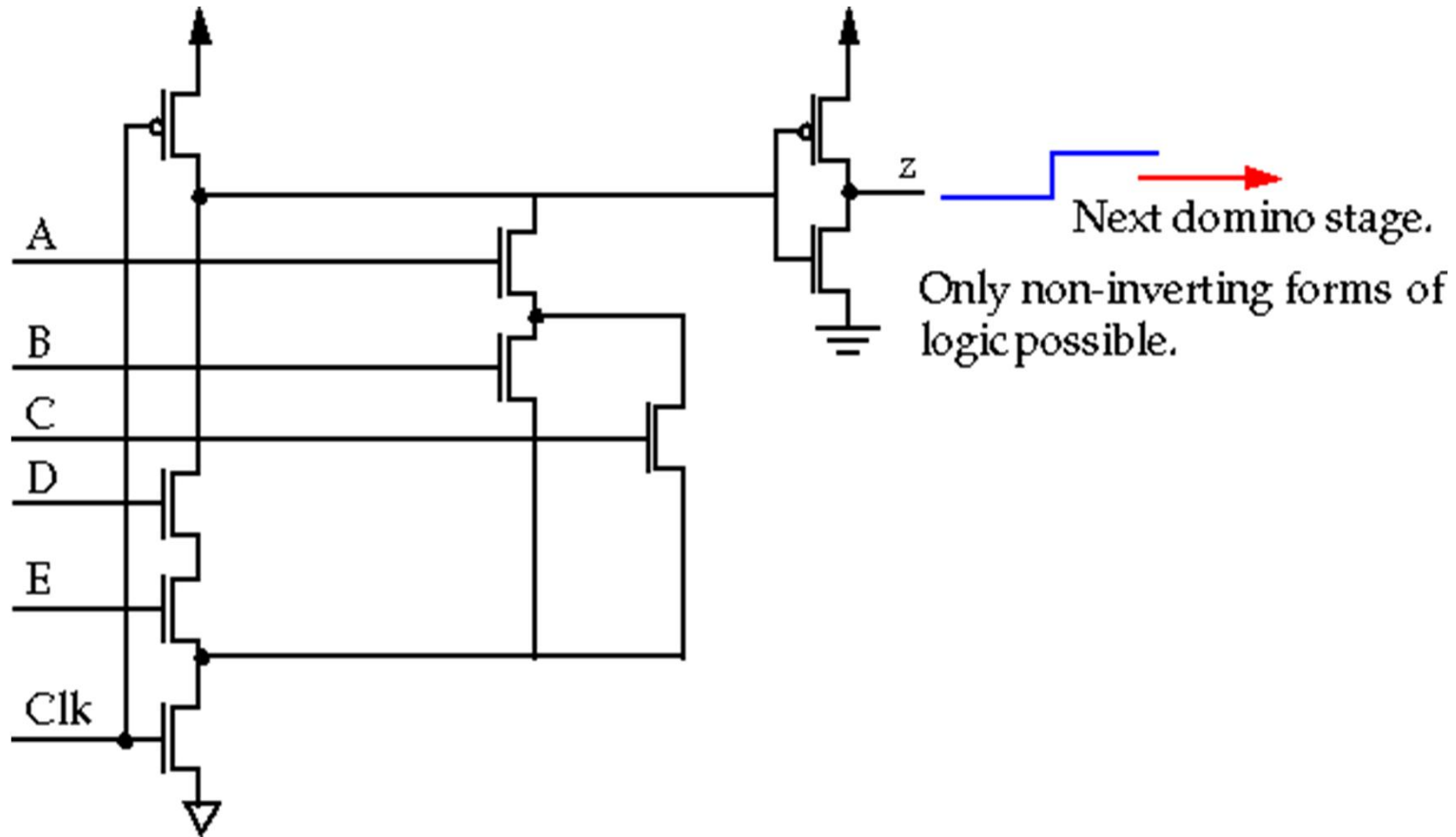

  
 
 
# Dynamic Logic

- *Dynamic* gates uses a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*



  
 
# The Foot

- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.


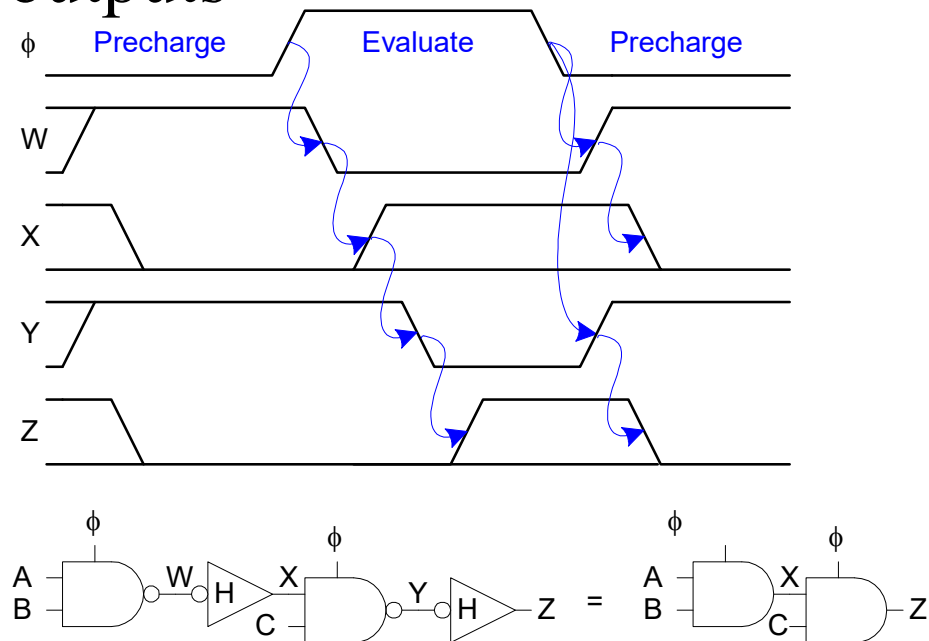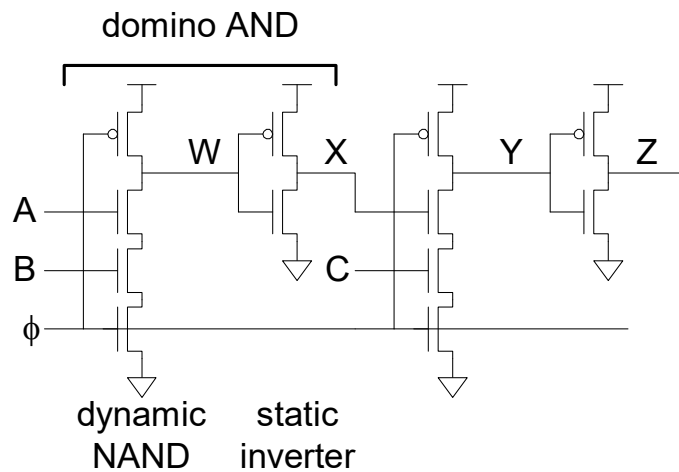
# Domino Gates

- Follow dynamic stage with inverting static gate
  - Dynamic / static pair is called domino gate
  - Produces monotonic outputs




# Dual-Rail Domino

---

- Domino only performs noninverting functions:
  - AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
  - Takes true and complementary inputs
  - Produces true and complementary outputs

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

 

# Example: AND/NAND

---


- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = A * B, Y_l = \sim(A * B)$


 
# Example: AND/NAND

---


- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = A * B, Y_l = \sim(A * B)$
- Pulldown networks are conduction complements


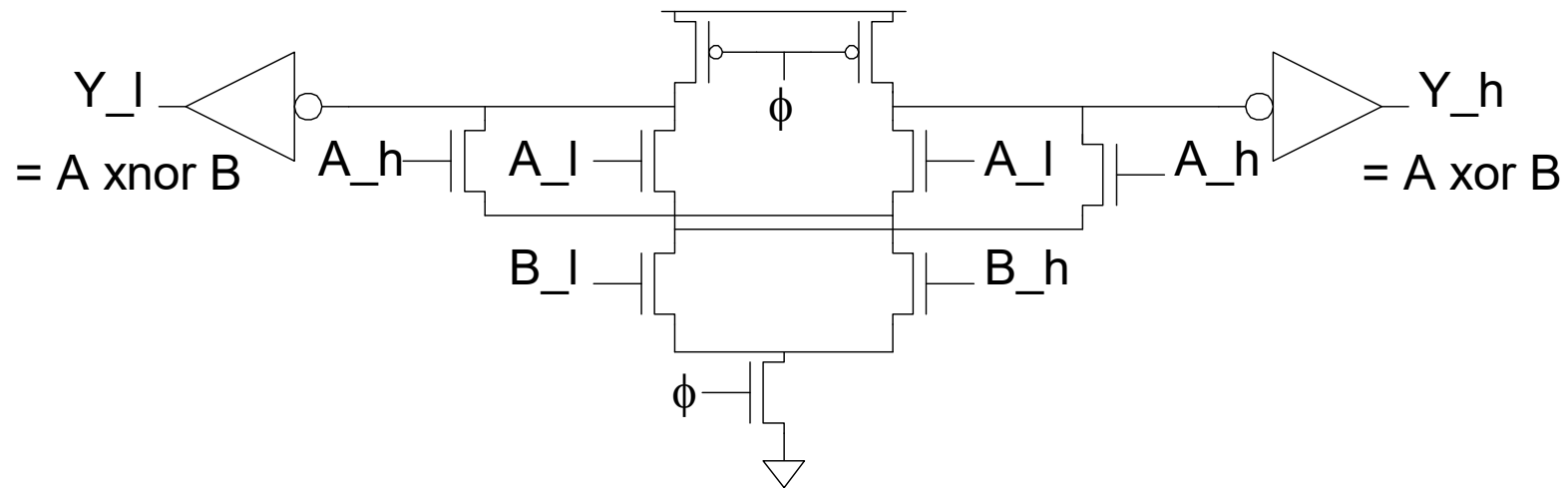
# Example: XOR/XNOR

---



- Sometimes possible to share transistors



  
# Pass Transistor Circuits

---

- Use pass transistors like switches to do logic
- Inputs drive diffusion terminals as well as gates
- CMOS + Transmission Gates:
  - 2-input multiplexer
  - Gates should be restoring



# Pass Transistor Logic

 

## XOR Truth Table

A	B	A xor B
0	0	0
0	1	1
1	0	1
1	1	0

## P

Pass function

$$\neg A + \neg B$$

$$\neg A + B$$

$$A + \neg B$$

$$\neg A + \neg B$$

0	0	1
	A B	A $\neg B$
1	$\neg A$ B	$\neg A \neg B$

